

ECE 182 Lab #2 Low Pass Filters

Day of Submission:09/12/2025

Name of student: Frank Tamburro

Circuit Design and Schematic

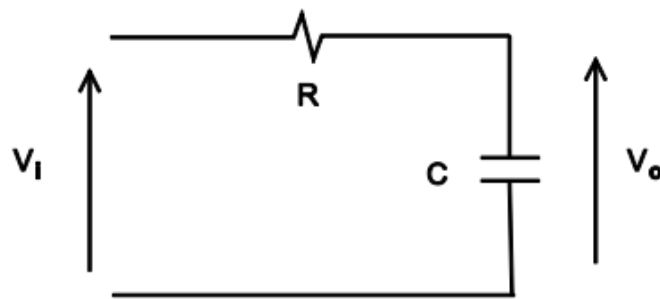


Fig 1 First order passive filter

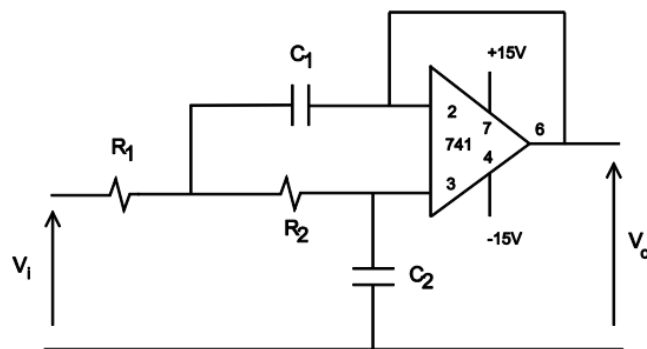


Fig 2 Second order active filter

Figure 1

- Theoretical vs Experimental Value
- R : 159.15ohm = 147.96ohm
- C : 1microfarad = 0.9696 microfarad

Figure 2

- Theoretical vs Experimental Value
- R_1 : 159.15ohm = 147.96ohm
- R_2 : 182.40ohm = 179.80ohm
- C_1 : 1microfarad = 0.9696 microfarad
- C_2 : 1microfarad = 0.9688 microfarad

Equations for Theoretical Basis

Figure 1 Magnitude Response Equation

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{6970.48}\right)^2}}$$

Figure 2 Magnitude Response Equation

$$|H(j\omega)| = \frac{1}{\sqrt{\left(1 - \frac{\omega}{(6325.86)^2}\right)^2 + \left(\frac{\omega}{3149.27}\right)^2}}$$

Results and Calculations

Figure 1 and 2 on Breadboard

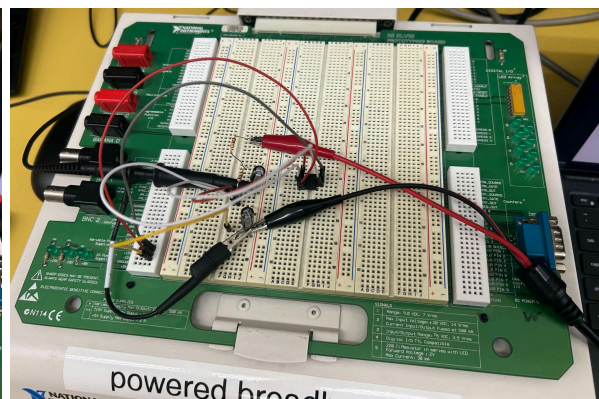
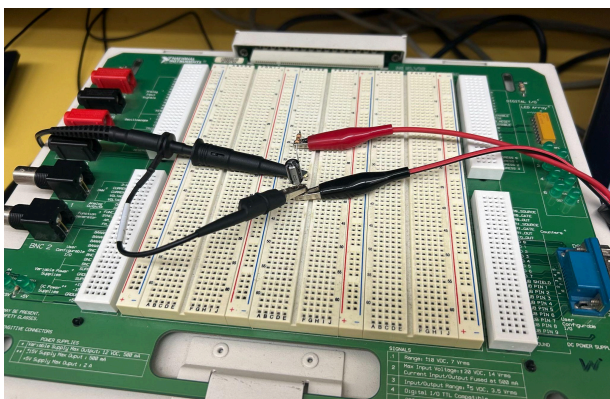


Figure 1 and 2 Data and Graphs

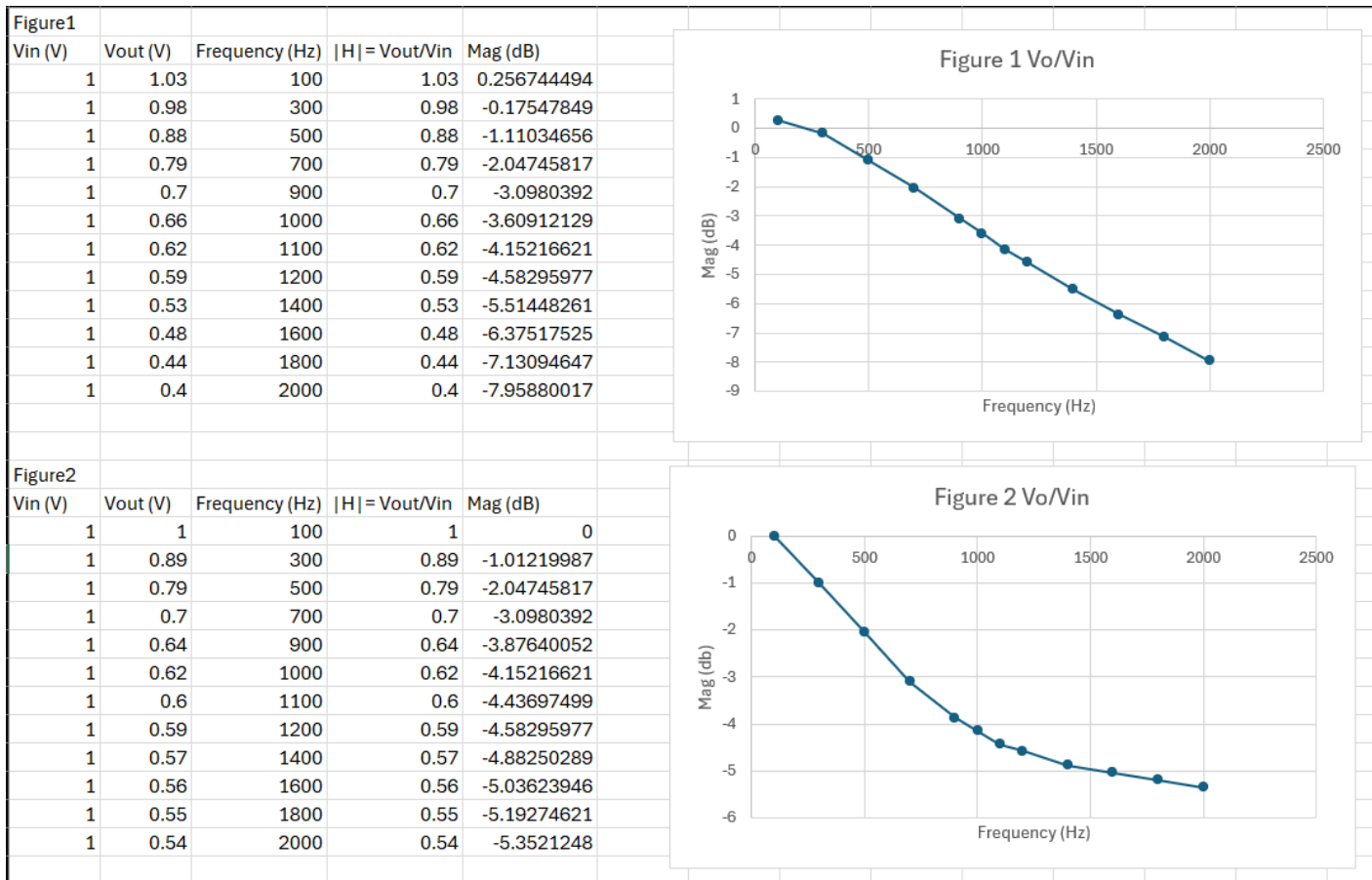


Figure 1 Calculations


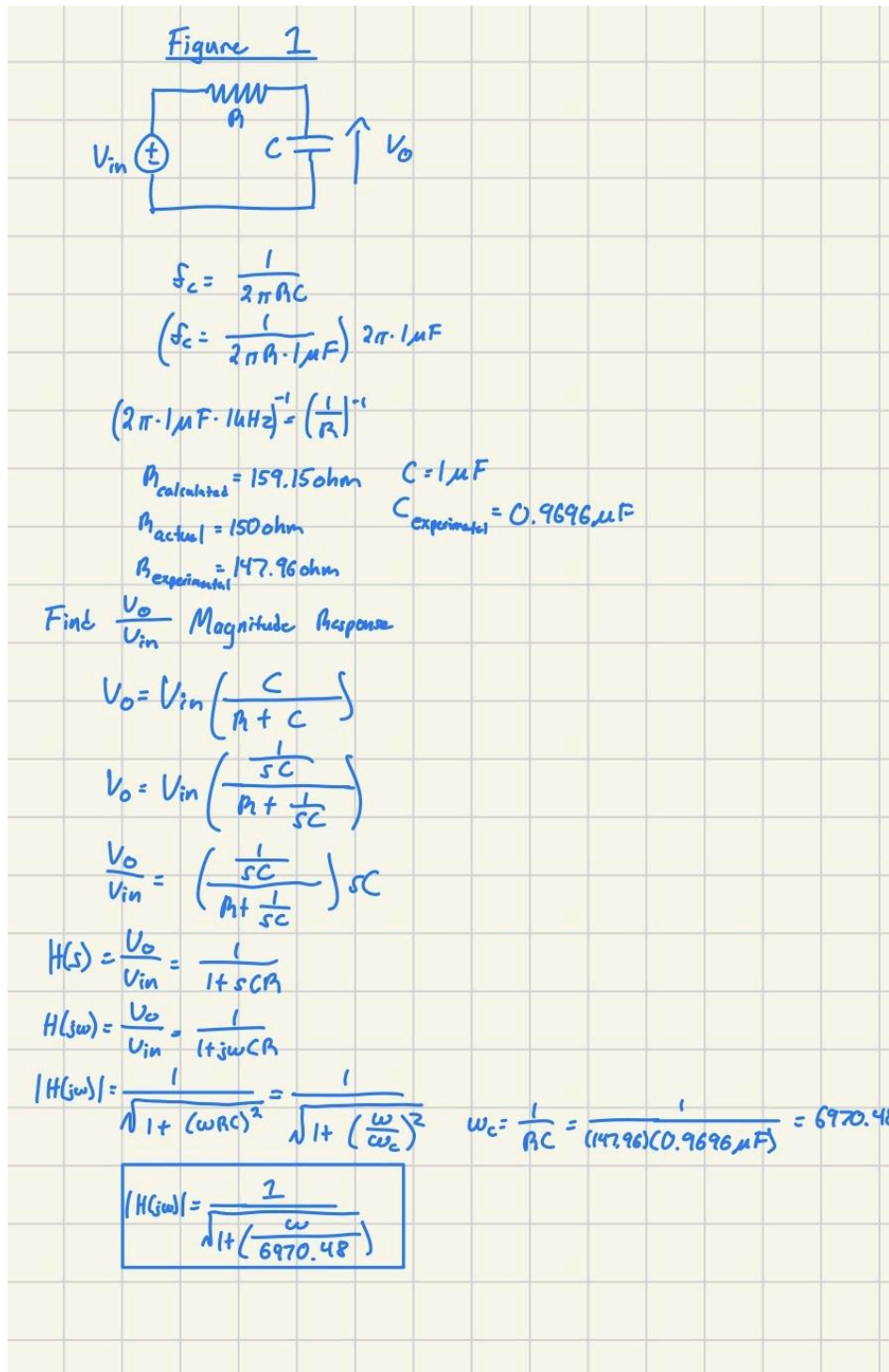


Figure 2 Calculations

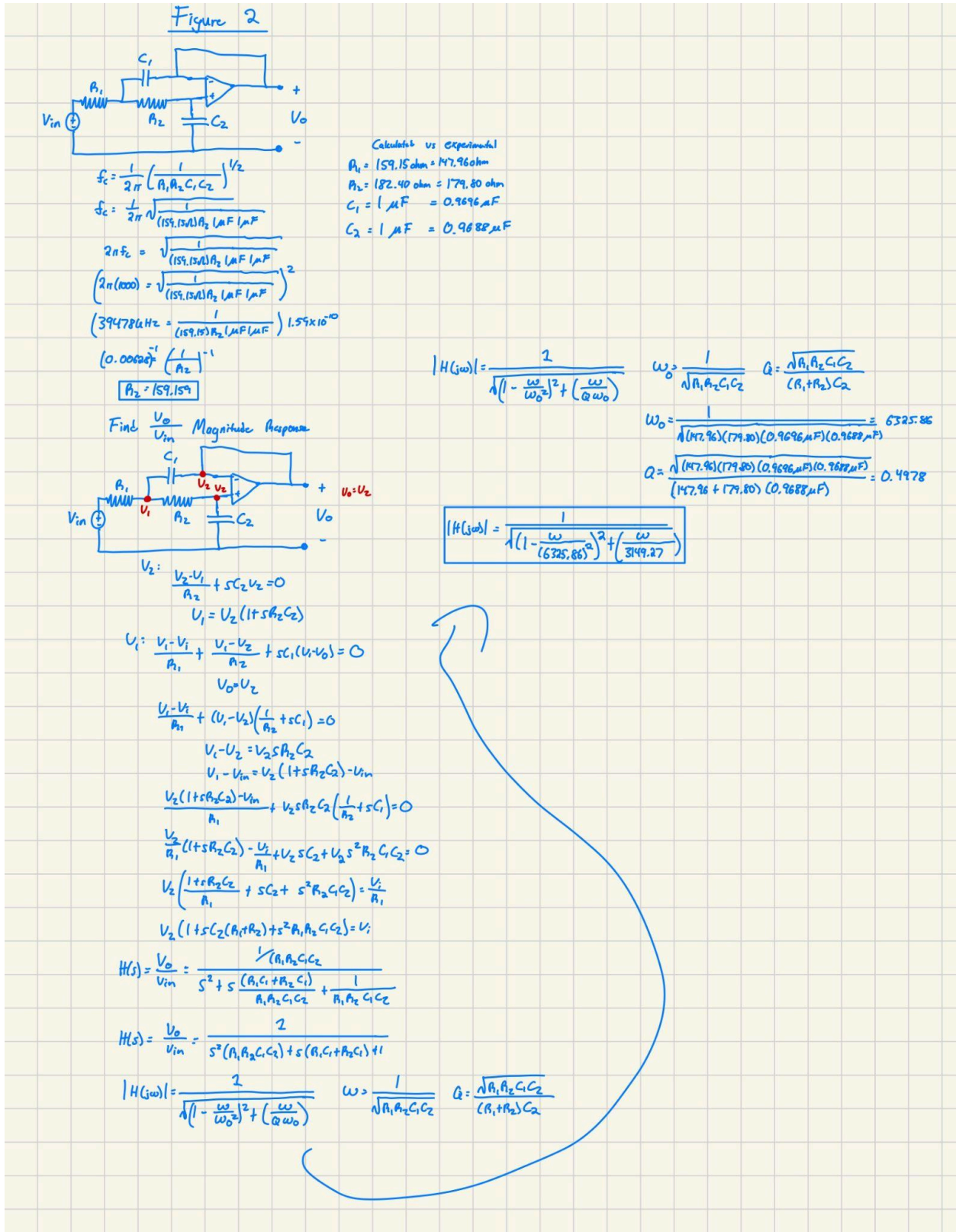

Summary

For the first order RC low pass filter which was designed to have a cutoff frequency of 1kHz. With the measured resistance being around 148 ohms and the capacitor being 0.9696 microfarads, theoretically $f_c = 1/(2\pi RC)$ should be around 1.1kHz. The reason for the increase in cutoff frequency is caused by the lab not having a 159.15 ohm resistor which would have been exactly 1kHz cutoff frequency. However the -3db cutoff was around 0.9/1KHz which corresponds with our theory. For the Sallen and Key low pass filter theory predicts cutoff frequency to be near 1kHz. The measured response matched this behavior, but the actual cutoff frequency from what we tested was around 700Hz. This lower cutoff frequency could have been caused by component tolerances, source calibration, or parasitic effects. However, our data overall matched our theory even with higher than expected error due to lab equipment and not having proper resistors.