

ECE 182 Lab #1 Instruments and Transients

Day of Submission:09/05/2025

Name of student: Frank Tamburro

Circuit Design and Schematic

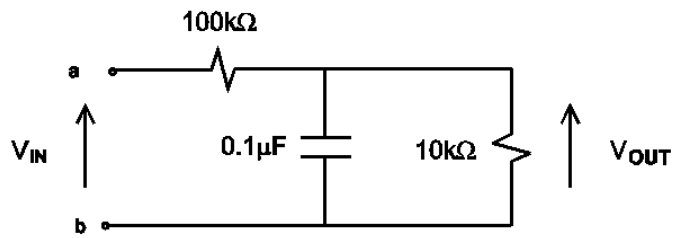


Fig. 1

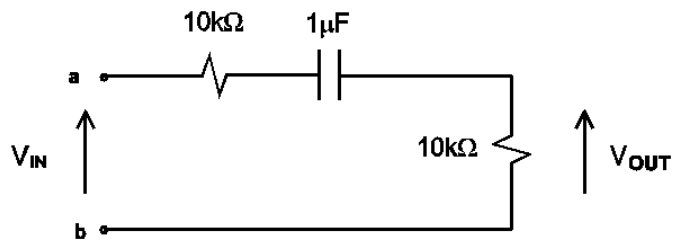


Fig. 2

Fig. 1

- Theoretical vs Experimental Value
- $100k\Omega = 98.123k\Omega$
- $10k\Omega = 9.857k\Omega$
- $0.1 \text{ microfarad} = 0.0992 \text{ microfarad}$

Fig. 2


- Theoretical vs Experimental Value
- $10k\Omega = 9.857k\Omega$
- $10k\Omega = 9.857k\Omega$
- $1 \text{ microfarad} = 0.9709 \text{ microfarad}$

Equations for Theoretical Basis



$$\text{Equation: } V_A(t) = V_f + (V_0 - V_f)e^{-t/\tau}$$

Results and Calculations



Figure 1 and 2 Circuits on Breadboard

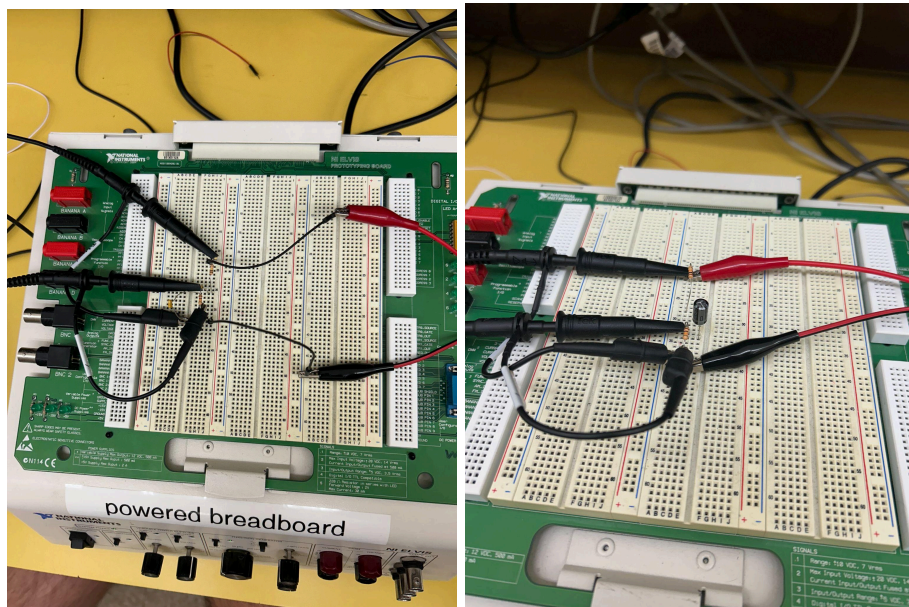

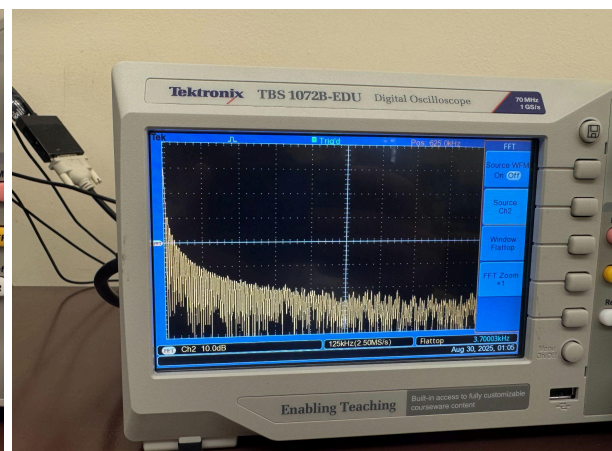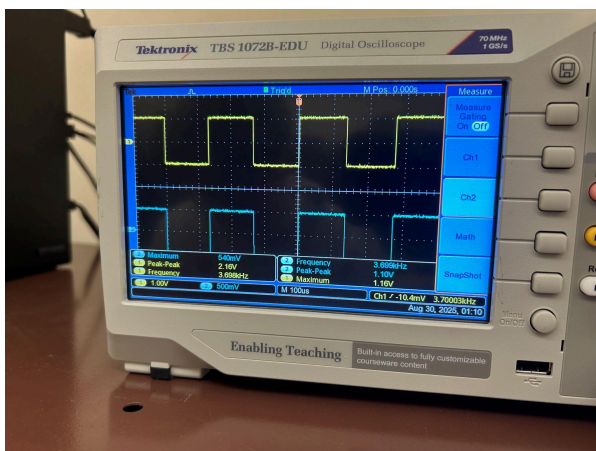
Left Image: Yellow Wave: Input, Blue Wave: Output. Right Image: FFT
Figure 1



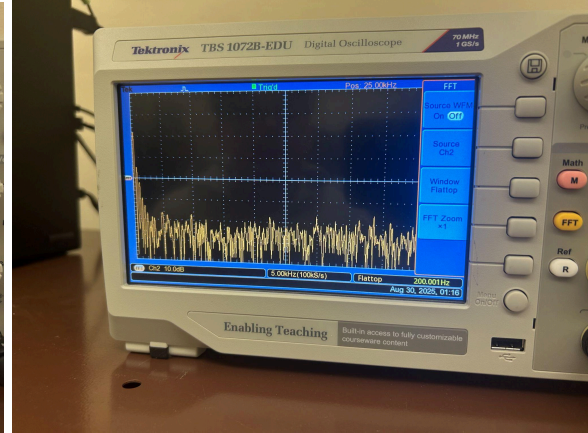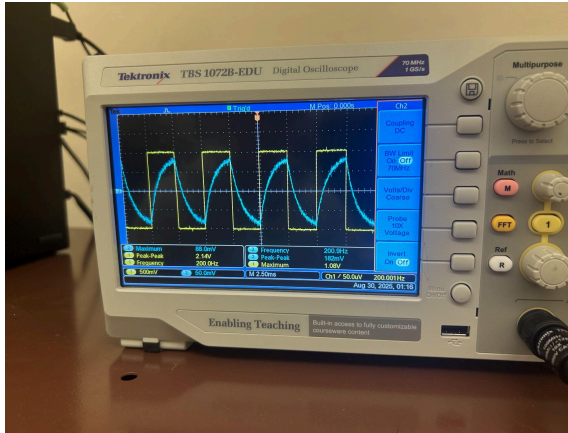Left Image: Yellow Wave: Input, Blue Wave: Output. Right Image: FFT
For Figure 2



Calculations for Figure 1 and 2

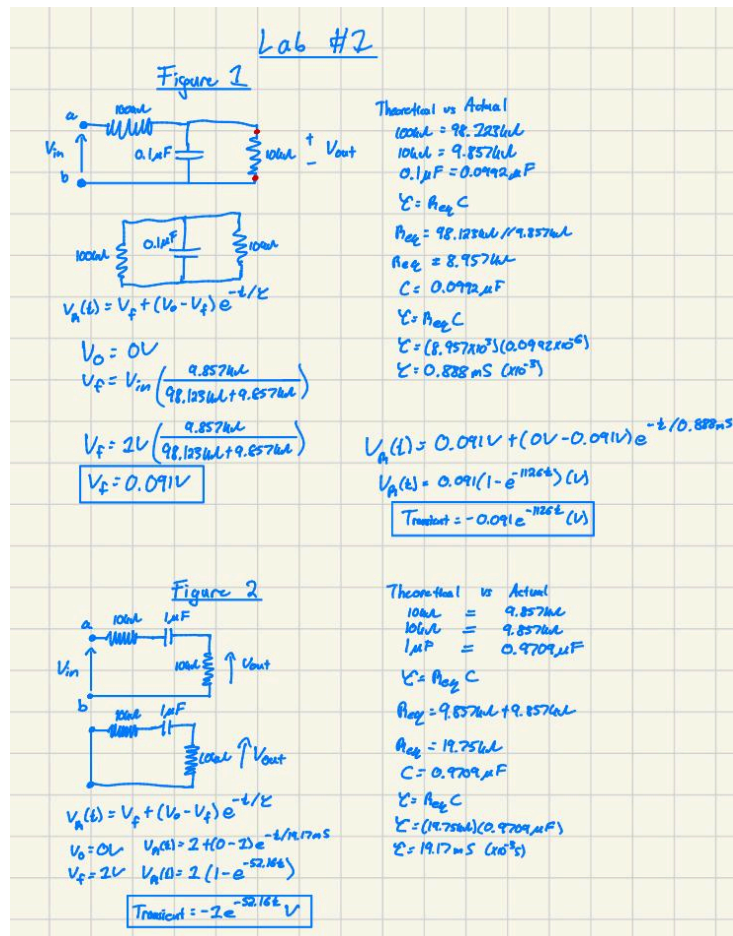

Summary

I built and tested Figure 1 (Low Pass Filter) and Figure 2 (High Pass Filter) with the input square waves and recorded output waves. I also recorded the FFT (Fast Fourier Transform) of both circuits to compare the theory and measured values. With all of the data gathered I used the equation (above) to calculate the transient of both circuits. Overall the theoretical values I calculated were very similar to the FFT's that I captured with only minor discrepancies due to equipment error.