

ECE 182 Lab #4 Phasor Voltages

Day of Submission: 09/19/2025

Name of student: Frank Tamburro

Circuit and Schematic

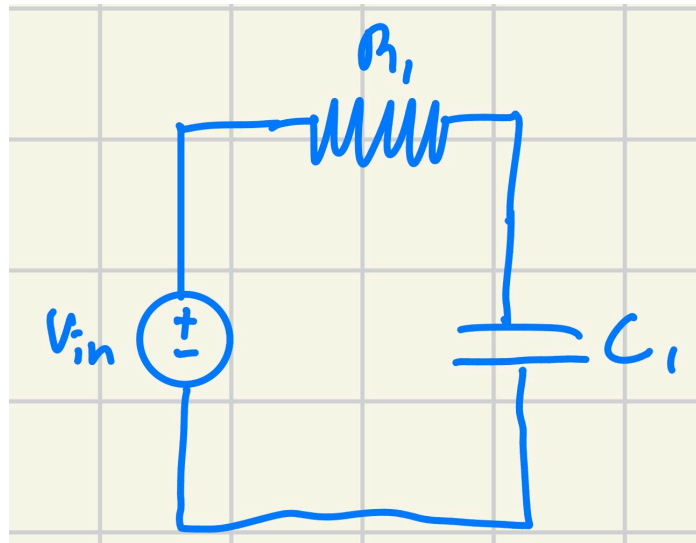


Figure 1

- Theoretical vs Experimental
- R1: 100 ohms vs 96.55 ohms
- C1: 22 farads vs 20.69 farads

Equations for Theoretical Basis

$$Z = R - jX_C \Rightarrow 96.55 - j 76.92 \Omega$$

Results and Calculations

Figure 1 on Breadboard



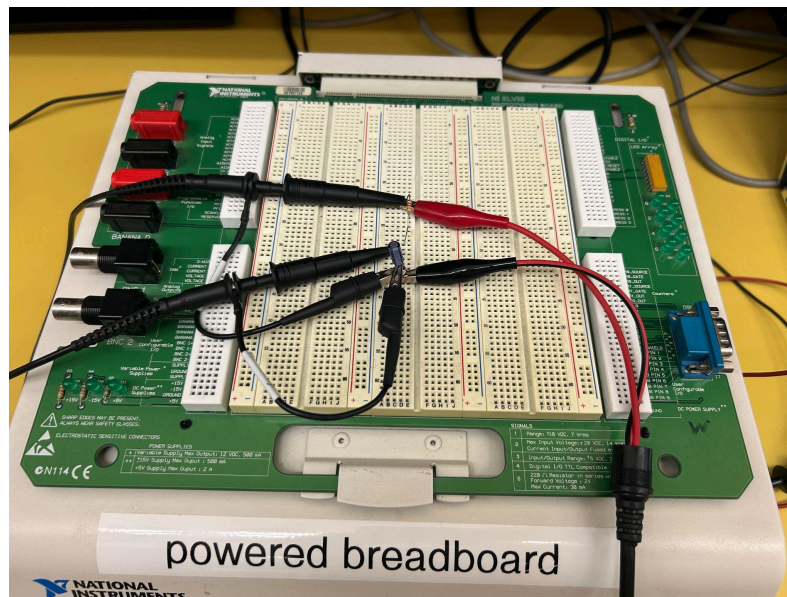


Figure 1 Measurements Yellow (Vin) vs Red (Resistor) vs Blue (Capacitor)

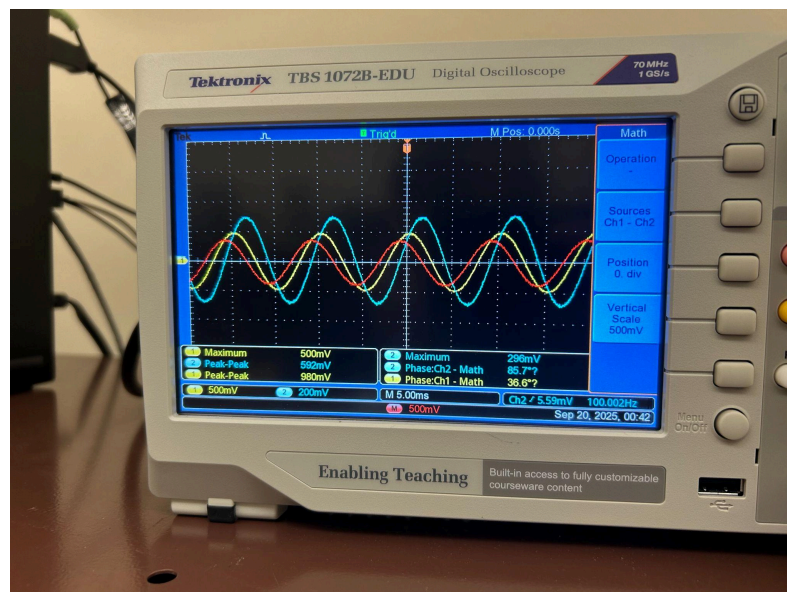

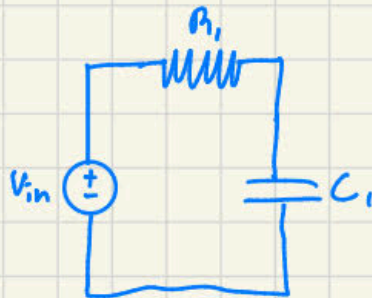

$$R_1 = 96.55 \text{ ohm}$$

$$C_1 = 20.69 \mu\text{F}$$

$$V_{in} = 3 \angle 0^\circ \text{ V} \quad 100 \text{ cycles/second}$$

$$\omega = 2\pi f = 200\pi$$

$$v(t) = V_m \cos(\omega t + \phi)$$

$$v(t) = \cos(200\pi t) \text{ V}$$

$$X_C = \frac{1}{j\omega C} = \frac{1}{(200\pi)(20.69 \times 10^{-6})} = 76.92 \Omega$$

$$R = 96.55 \text{ ohm}$$

$$Z = R - jX_C = 96.55 - j76.92 \Omega$$

$$Z = 123.44 \angle -38.54^\circ$$

$$V = IZ \Rightarrow I = \frac{V}{Z}$$

$$I = \frac{3 \angle 0^\circ}{123.44 \angle -38.54^\circ}$$

$$I = 8.101 \angle 38.54^\circ \text{ mA}$$

$$V_R = IR$$

$$V_R = 8.101 \angle 38.54^\circ \text{ mA} \cdot 96.55 \Omega$$

$$V_R = 0.782 \angle 38.54^\circ \text{ V}$$

$$|Z| = \sqrt{R^2 + X_C^2}$$

$$|Z| = \sqrt{(96.55)^2 + (76.92)^2}$$

$$|Z| = 123.44$$

$$\phi = \tan^{-1}\left(\frac{-76.96}{96.55}\right)$$

$$\phi = -38.54^\circ$$

$$V_C = IZ_C$$

$$V_C = 8.101 \angle 38.54^\circ \text{ mA} \cdot (-jX_C)$$

$$V_C = 8.101 \angle 38.54^\circ \text{ mA} \cdot 76.923 \angle -90^\circ$$

$$V_C = 0.623 \text{ V} \angle -51.46^\circ$$

Yellow = V_{in}

Red = Resistor = 36.6°

Blue = Capacitor = 85.7°

$$\begin{array}{r} 36.6^\circ \\ -85.7^\circ \\ \hline -49.1 \end{array}$$

Experimental	$V_R \angle \theta$	$V_C \angle \theta$
	$0.50 \text{ V} \angle 36.6^\circ$	$0.592 \text{ V} \angle -49.1^\circ$
Theoretical	$V_R \angle \theta$	$V_C \angle \theta$
	$0.782 \text{ V} \angle 38.59^\circ$	$0.623 \text{ V} \angle -51.46^\circ$

Summary

The measured phasor voltage confirmed the expected RC circuit behavior, with resistor voltage nearly in phase with the input and the capacitor voltage lagging close to 90 degrees. The overall phase/amplitude relationships matched theoretical predictions (V_r Experimental = $0.50V \angle 36.6^\circ$ and Theoretical $0.782V \angle 38.59^\circ$, V_c Experimental = $0.592V \angle -49.1^\circ$ and Theoretical = $0.623V \angle -51.47^\circ$), with only minor deviations due to component tolerances and measurement error. The resistor measured 96.55 ohms vs the expected 100 ohms, and the capacitor measured 20.69 micro farads vs the expected 22 micro farads. These minor differences lead to small shifts in the observed voltages. Overall, the lab was a success because the experimental data closely followed the expected phasor analysis and validated the theoretical model.